

9 Transmission Lines

9.1 Introduction

1. EM wave in free space and in waveguides or transmission lines
2. Examples of transmission lines
 - two-wire lines
 - coaxial cable
 - metal interconnection in PCB or IC

9.3 General Transmission Line Equations

1. Electric circuit: $\ell \ll \lambda$, no current/voltage variation in lumped elements

Transmission line: $\ell \gg, \geq \lambda$, distributed circuit elements

2. Distributed model of transmission lines

Consider a differential length Δz of a general two conductor transmission line (parallel plate, coaxial cables, etc.) described by

$$\left\{ \begin{array}{l} R = \text{resistance per unit length of the conductors } (\Omega/\text{m}) \\ L = \text{inductance per unit length of the line } (\text{H}/\text{m}) \\ G = \text{conductance per unit length of the dielectric medium } (\text{S}/\text{m}) \\ C = \text{capacitance per unit length of the line } (\text{F}/\text{m}) \end{array} \right.$$

(see Tables 9-1 and 9-2)

3. Applying Kirchhoff's voltage law, we have

4. Applying Kirchhoff's current law at node N, we have

((9-31) and (9-33) are the general transmission line equations (telegrapher's equations)

5. In phasor form,

$$\Rightarrow \begin{cases} v(z, t) = \Re[V(z)e^{j\omega t}] \\ i(z, t) = \Re[I(z)e^{j\omega t}] \\ -\frac{dV(z)}{dz} = (R + j\omega L)I(z) \\ -\frac{dI(z)}{dz} = (G + j\omega C)V(z) \end{cases} \quad (9-35)$$

- time harmonic transmission line equation

- In circuit theory, Fourier transform reduces an ordinary differential equation to an algebraic equation.

In EM and transmission line theory, Fourier transform reduces a partial differential equation to an ordinary differential equation.

9.3.1 Wave on an Infinite Transmission Line

1. Decoupled wave equations:

$$\text{where } \begin{cases} \gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)} = \text{propagation constant} \\ \alpha = \text{attenuation constant} \\ \beta = \text{phase constant} \end{cases}$$

2. Solution of the wave equations:

For an infinite line, only $V^+(z)$ and $I^+(z)$ exist (no reflection)

$$\begin{cases} V(z) = V^+(z) = V_0^+ e^{-\gamma z} \\ I(z) = I^+(z) = I_0^+ e^{-\gamma z} \\ Z_0 \triangleq \frac{V(z)}{I(z)} = \frac{V_0^+}{I_0^+} = \text{constant} \end{cases}$$

$\Rightarrow Z_0 =$ characteristic impedance of the line (independent of length)

Ex 9-2: Analogy between waves on a transmission line and in a dielectric medium

- For a uniform plane wave with E_x and H_y only, the Maxwell's equations can be reduced to

$$\begin{cases} \nabla \times \mathbf{E} = -j\omega(\mu' - j\mu'')\mathbf{H} \\ \nabla \times \mathbf{H} = j\omega(\epsilon' - j\epsilon'')\mathbf{E} \end{cases} \Rightarrow \begin{cases} -\frac{dE_x(z)}{dz} = (\omega\mu'' + j\omega\mu')H_y(z) \\ -\frac{dH_y(z)}{dz} = (\omega\epsilon'' + j\omega\epsilon')E_x(z) \end{cases}$$

$$\Rightarrow \begin{cases} E_x \leftrightarrow V \\ H_y \leftrightarrow I \end{cases} \text{ and } \begin{cases} R \leftrightarrow \omega\mu'' \\ L \leftrightarrow \mu' \\ G \leftrightarrow \omega\epsilon'' \\ C \leftrightarrow \epsilon' \end{cases}$$

$$\gamma = \alpha + j\beta = \omega\sqrt{\mu\epsilon} = \sqrt{(\omega\mu'' + j\omega\mu')(\omega\epsilon'' + j\omega\epsilon')}$$

$$Z_0 \leftrightarrow \eta_c = \sqrt{\frac{\mu'' + j\mu'}{\epsilon'' + j\epsilon'}}$$

- Reflection from interface or discontinuity

3. Characteristic impedance and propagation constant

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

$$\gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)}$$

(a) lossless lines ($R = 0, G = 0$)

$$\gamma = j\omega\sqrt{LC}, \alpha = 0, \beta = \omega\sqrt{LC}$$

$$u_p = \omega/\beta = 1/\sqrt{LC}$$

$$Z_0 = R_0 + jX_0 = \sqrt{L/C} \Rightarrow \begin{cases} R_0 = \sqrt{L/C} = \text{constant} \\ X_0 = 0 \end{cases}$$

(b) low loss lines ($R \ll \omega L, G \ll \omega C$)

$$\Rightarrow \alpha \approx \frac{1}{2} \left(R\sqrt{\frac{C}{L}} + G\sqrt{\frac{L}{C}} \right)$$

$$\beta \approx \omega\sqrt{LC}$$

$$u_p = \omega/\beta \approx 1/\sqrt{LC} \text{ (approximately constant)}$$

$$Z_0 = R_0 + jX_0 \approx \sqrt{\frac{L}{C}} \left(1 + \frac{1}{j2\omega} \left(\frac{R}{L} - \frac{G}{C} \right) \right)$$

$$\Rightarrow R_0 \approx \sqrt{\frac{L}{C}},$$

$$X_0 \approx \sqrt{\frac{L}{C}} \frac{1}{2\omega} \left(\frac{R}{L} - \frac{G}{C} \right) \rightarrow 0 \text{ for low loss lines}$$

(c) distortionless (dispersionless) lines ($\frac{R}{L} = \frac{G}{C}$)

$$\Rightarrow \alpha = R\sqrt{\frac{C}{L}} = \text{constant}$$

$$\beta = \omega\sqrt{LC}$$

$$u_p = \omega/\beta = 1/\sqrt{LC} = \text{constant} \Rightarrow \text{no distortion}$$

$$Z_0 = \dots = \sqrt{L/C}$$

$$\Rightarrow R_0 = \sqrt{L/C}, X_0 = 0$$

Ex 9-3: 50Ω Distortionless lines

9.4 Wave on Finite Transmission Lines

1. For a general transmission line,

$$\begin{cases} V(z) = V_0^+ e^{-\gamma z} + V_0^- e^{+\gamma z} \\ I(z) = \underbrace{I_0^+ e^{-\gamma z}}_{+z \text{ wave}} + \underbrace{I_0^- e^{+\gamma z}}_{-z \text{ wave}} \end{cases}$$

$$\frac{V_0^+}{I_0^+} = -\frac{V_0^-}{I_0^-} = Z_0 = \text{characteristic impedance}$$

2. Now consider a finite line (Z_0) terminated with a load impedance Z_L ,

at $z = \ell$, V and I must satisfy

- (a) If $Z_L = Z_0$ (matched line) \Rightarrow no backward (reflected) wave
- (b) If $Z_L \neq Z_0$ (unmatched line) \Rightarrow a reflected wave must exist in order to satisfy the above boundary condition

3. $V(z)$ and $I(z)$ can be expressed in terms of V_i, I_i or V_L, I_L :

$$\begin{cases} V(\ell) = V_L = V_0^+ e^{-\gamma \ell} + V_0^- e^{+\gamma \ell} \\ I(\ell) = I_L = \frac{V_0^+}{Z_0} e^{-\gamma \ell} - \frac{V_0^-}{Z_0} e^{+\gamma \ell} \end{cases}$$

$$\Rightarrow \begin{cases} V_0^+ = \frac{1}{2}(V_L + I_L Z_0) e^{\gamma \ell} \\ V_0^- = \frac{1}{2}(V_L - I_L Z_0) e^{-\gamma \ell} \end{cases}$$

Let $z' = \ell - z =$ distance backward from the load

$$\begin{cases} V(z') = \frac{I_L}{2} [(Z_L + Z_0) e^{\gamma z'} + (Z_L - Z_0) e^{-\gamma z'}] \\ I(z') = \frac{I_L}{2Z_0} \underbrace{[(Z_L + Z_0) e^{\gamma z'}]}_{-z' \text{ wave}} - \underbrace{[(Z_L - Z_0) e^{-\gamma z'}]}_{+z' \text{ wave}} \end{cases}$$

$$\text{Or, } V(z') = \frac{I_L}{2} [Z_L(e^{\gamma z'} + e^{-\gamma z'}) + Z_0(e^{\gamma z'} - e^{-\gamma z'})]$$

\Rightarrow

$$\Rightarrow Z(z') = \frac{V(z')}{I(z')} = \text{impedance at } z' \text{ looking toward the load}$$

4. At the source, $z' = \ell$,

Z_i = input impedance seen by the generator

\Rightarrow equivalent circuit

5. Average power delivered by the generator to the line:

$$(P_{\text{av}})_i = \frac{1}{2} \Re[V_i I_i^*] |_{z=0, z'=\ell}$$

Average power delivered to the load

$$(P_{\text{av}})_L = \frac{1}{2} \Re[V_L I_L^*] |_{z=\ell, z'=0} = \frac{1}{2} \left| \frac{V_L}{Z_L} \right|^2 R_L = \frac{1}{2} I_L^2 R_L$$

(for lossless lines, $(P_{\text{av}})_i = (P_{\text{av}})_L$)

6. If $Z_L = Z_0$ (matched),

\rightarrow (9-98) is reduced to

$$\begin{cases} V(z) = V_i e^{-\gamma z} \\ I(z) = V_i e^{-\gamma z} \end{cases}$$

\Rightarrow no reflection wave, similar to infinite line

Ex 9-5: 50Ω lossless matched line

(a) instantaneous V and I at arbitrary locations

(b) instantaneous V and I at load

(c) average power to the load

9.4.1 Transmission Lines as Circuit Elements

1. At UHF, $f = 300 \text{ MHz} \sim 3 \text{ GHz}$, $\lambda = 1 \text{ m} \sim 0.1 \text{ m}$. Lumped elements are difficult to make (stray field effect).

\Rightarrow finite transmission line can be used as circuit elements.

2. Consider a lossless transmission line segment,

$$Z(z') = Z_0 \frac{Z_L + Z_0 \tanh \gamma z'}{Z_0 + Z_L \tanh \gamma z'}$$

(a) $Z_L \rightarrow \infty$ (open circuit termination)

(Note: It is difficult to obtain $Z_L \rightarrow \infty$ due to field coupling and radiation.)

(b) $Z_L = 0$ (short circuit termination)

(c) Quarter wave section ($\ell = \lambda/4, \beta\ell = \pi/2$)

or $\ell = (2n - 1)\lambda/4, n = 1, 2, 3, \dots, \Rightarrow \tan \beta\ell = \pm\infty$

\Rightarrow

(d) Half wave section ($\ell = \lambda/2, \beta\ell = \pi$)

or $\ell = n\lambda/2, n = 1, 2, 3, \dots, \Rightarrow \tan \beta\ell = 0$

$\Rightarrow Z_i = Z_L$ (why?)

3. By measuring $Z_{io} = Z_0 \coth \gamma\ell$ and $Z_{is} = Z_0 \tanh \gamma\ell$, we can determine

$$Z_0 = \sqrt{Z_{io}Z_{is}} \quad (\Omega)$$

$$\gamma = \frac{1}{\ell} \tanh^{-1} \sqrt{\frac{Z_{is}}{Z_{io}}} \quad (\text{m}^{-1})$$

Ex 9-6: Open- and short-circuited impedance

(a)

(b)

(c)

9.4.2 Resistive Termination

1. For $z' = \ell - z$,

$$V(z') = \frac{I_L}{2} \left[\underbrace{(Z_L + Z_0)e^{\gamma z'}}_{-z' \text{ incident wave}} + \underbrace{(Z_L - Z_0)e^{-\gamma z'}}_{+z' \text{ reflected wave}} \right]$$

Similarly,

$$I(z') = \frac{I_L}{2Z_0} (Z_L + Z_0)e^{\gamma z'} (1 - \Gamma e^{-2\gamma z'})$$

2. For lossless lines, $\gamma = j\beta$, $Z_0 = R_0$,

$$\begin{cases} V(z') = \frac{I_L}{2}(Z_L + R_0)e^{j\beta z'}(1 + |\Gamma|e^{j(\theta_\Gamma - 2\beta z')}) \\ I(z') = \frac{I_L}{2R_0}(Z_L + R_0)e^{j\beta z'}(1 - |\Gamma|e^{j(\theta_\Gamma - 2\beta z')}) \end{cases} \quad (9 - 135)$$

Or from (9-100, p. 9-6) and $V_L = I_L Z_L$, $Z_L = R_L$ (purely resistive load)

$$\begin{cases} |V(z')| = V_L \sqrt{\cos^2 \beta z' + (R_0/R_L)^2 \sin^2 \beta z'} \\ |I(z')| = I_L \sqrt{\cos^2 \beta z' + (R_0/R_L)^2 \sin^2 \beta z'} \end{cases} \quad (9 - 137)$$

3. Standing wave on transmission lines

(a) For $R_L = R_0$, or, in general, $Z_L = Z_0$, there is no reflected wave ($\Gamma = 0$) and $|V(z')| = V_L = \text{constant}$

(b) For $R_L \neq R_0$, or, in general, $Z_L \neq Z_0$, there is a reflected wave ($\Gamma \neq 0$) and $|V(z')| \neq \text{constant}$ due to the interference of the two waves

(Note: the period of the standing wave pattern is $\lambda/2$)

(c) The standing wave ratio is defined as

For a lossless line,

- $Z_L = Z_0$ (matched) $\Rightarrow \Gamma = 0, S = 1$
- $Z_L = 0$ (short circuited) $\Rightarrow \Gamma = -1, S \rightarrow \infty$
- $Z_L = \infty$ (open circuited) $\Rightarrow \Gamma = 1, S \rightarrow \infty$

4. max and min of V and I on the transmission line for general load

From (9-135),

$|V_{\max}|, |I_{\min}|$ occurs at $\theta_\Gamma - 2\beta z' = -2n\pi, n = 0, 1, 2, \dots$

$|V_{\min}|, |I_{\max}|$ occurs at $\theta_\Gamma - 2\beta z' = -(2n + 1)\pi, n = 1, 2, \dots$

For resistive termination on a lossless line, both Z_L and Z_0 are real,

$$(1) R_L > R_0, \theta_\Gamma = 0$$

$$(2) R_L < R_0, \theta_\Gamma = \pi$$

9.4.3 Arbitrary Termination (see Smith Chart)

9.4.4 Transmission Line Circuit

1. To express $V(z')$ in terms of V_g , let us consider the multiple reflections at $z = 0$ and $z = \ell$:

$$\begin{aligned} V(z') &= \sum \text{all waves traveling in the line} \\ &= V_1^+ + V_1^- + V_2^+ + V_2^- + \dots \\ &= \end{aligned}$$

If $Z_L = Z_0 \Rightarrow$ only V_1^+ exists ($\Gamma = 0$)

If $Z_L \neq Z_0$ but $Z_g = Z_0 \rightarrow \Gamma \neq 0, \Gamma_g = 0 \Rightarrow$ only V_1^+ and V_1^- exist

Ex 9-10: 50Ω lossless air line

9.6 Smith Chart

1. For a lossless line, the reflection coefficient Γ is

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{Z_L - R_0}{Z_L + R_0} = |\Gamma|e^{j\theta_r}$$

2. If the load impedance is normalized to the line impedance R_0 ,

It can be shown that

$$\begin{cases} r = \frac{1 - \Gamma_r^2 - \Gamma_i^2}{(1 - \Gamma_r)^2 + \Gamma_i^2} \\ x = \frac{2\Gamma_i}{(1 - \Gamma_r)^2 + \Gamma_i^2} \end{cases}$$

3. The real part of the normalized load impedance r can be plotted in the complex Γ plane. It can be shown that

$$\Rightarrow \text{circle centered at } (\Gamma_r, \Gamma_i) = \left(\frac{r}{1+r}, 0\right) \text{ with radius} = \frac{1}{1+r}$$

Similarly, the imaginary part x satisfies

$$\Rightarrow \text{circle centered at } \left(1, \frac{1}{x}\right) \text{ with radius} = \frac{1}{x}$$

- (a) Constant- r circles (Eq. 9-188):
- i. centered on the Γ_r axis ($\Gamma_i = 0$)
 - ii. largest circle: $r = 0$ centered at $(0, 0)$
 - iii. for $r \rightarrow \infty$, r -circle $\rightarrow (1, 0)$ (open circuit)
 - iv. all r -circles pass through $(1, 0)$
- (b) Constant- x circles (Eq. 9-189):
- i. centered on the $\Gamma_r = 1$ line
 - ii. for $x = 0 \Rightarrow \Gamma_r$ axis
 - iii. for $x = 0 \rightarrow \infty$, x -circle $\rightarrow (1, 0)$ (open circuit)
 - iv. all x -circles pass through $(1, 0)$

4. Smith Chart:

- (a) r - and x -circles are plotted in $\Gamma_r - \Gamma_i$ plane for $|\Gamma| \leq 1$;
- (b) Intersection of a r - and a x -circle represents a normalized load impedance $z_L = r + jx$.

Ex: In Fig. 9-30, the point P is found to be $(r, x) = (1.7, 0.6)$. Therefore, the normalized impedance is

and the real load impedance is

Some interesting points on the chart:


$$P_{SC} : (r, x) =$$

$$P_{OC} : (r, x) =$$

- (c) Once the point representing the normalized impedance is located, the reflection coefficient $\Gamma = |\Gamma|e^{j\theta_\Gamma}$ can be found from the chart, and vice versa.

The Complete Smith Chart

Black Magic Design

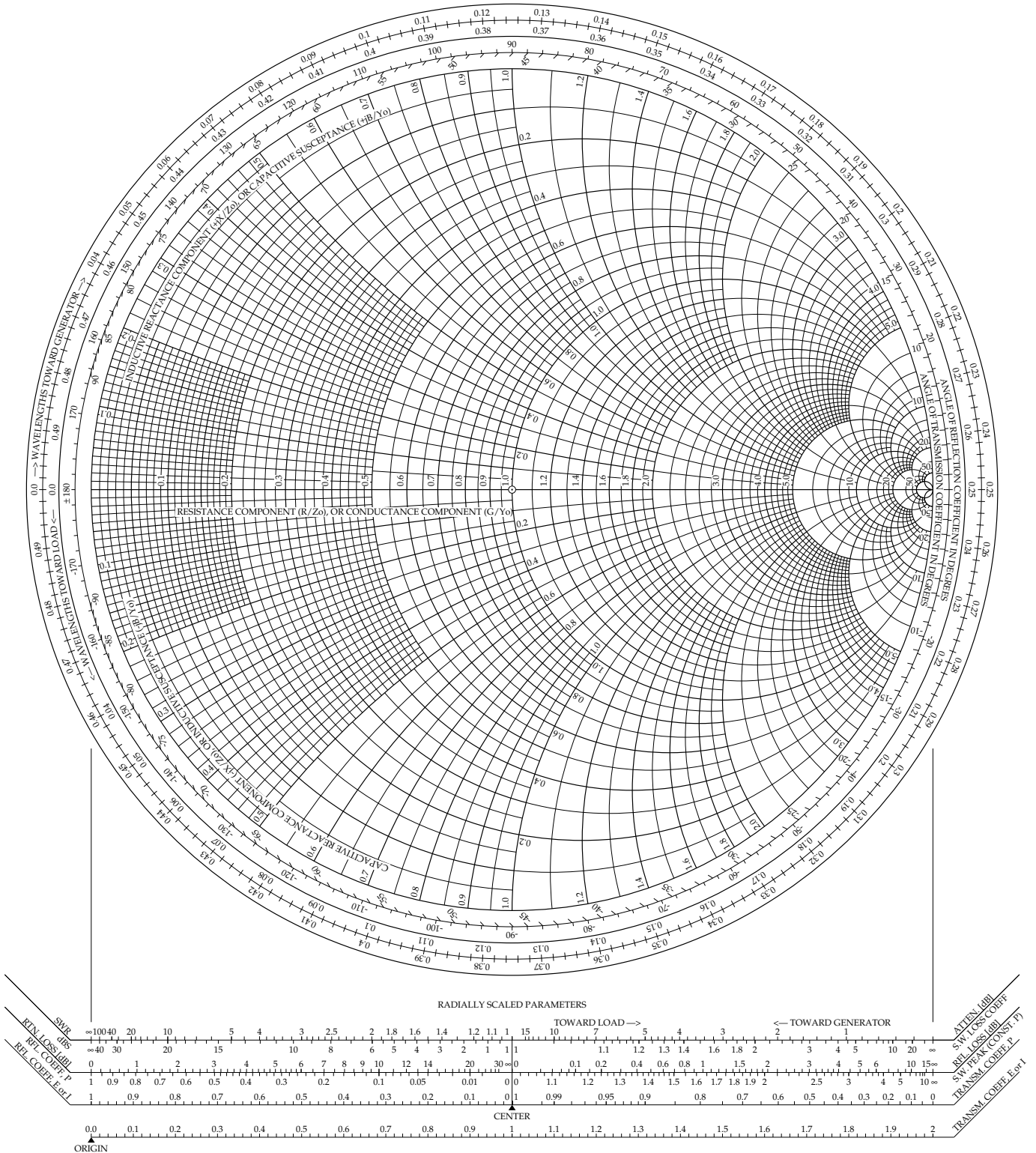

(Source: Wikipedia)

(d) Constant- $|\Gamma|$ circles:

- i. centered at $(0, 0)$ and $0 \leq |\text{radius}| \leq 1$
- ii. P_M, P_m :

\Rightarrow SWR=the r -circle passing through P_M

5. Input impedance calculation using Smith Chart

$$Z_i(z') = \frac{V(z')}{I(z')} = Z_0 \frac{1 + \Gamma e^{-j2\beta z'}}{1 - \Gamma e^{-j2\beta z'}} \quad (\text{Eq. 9-133, } \gamma = j\beta)$$

\Rightarrow on the Γ -plane (Smith chart), $z_i(z')$ is located on the $|\Gamma|$ -circle with phase angle $\phi = \theta_\Gamma - 2\beta'$

But $|\Gamma|$ and S are independent of z'


$\Rightarrow z_i(z')$ can be found from proper rotation of z_L on the $|\Gamma|$ -circle:

Given $z_L = z_i(0)$,

- (a) find $\Gamma = |\Gamma|e^{j\theta_\Gamma}$;
- (b) rotate the Γ point clockwise along the $|\Gamma|$ -circle by an angle of $2\beta z' = 4\pi z'/\lambda$ to Γ' (subtraction of phase)
- (c) $\Gamma' = |\Gamma|e^{j(\theta_\Gamma - 2\beta z')} = |\Gamma|e^{j\phi}$ corresponds to the input impedance z_i at z'

The Complete Smith Chart


Black Magic Design

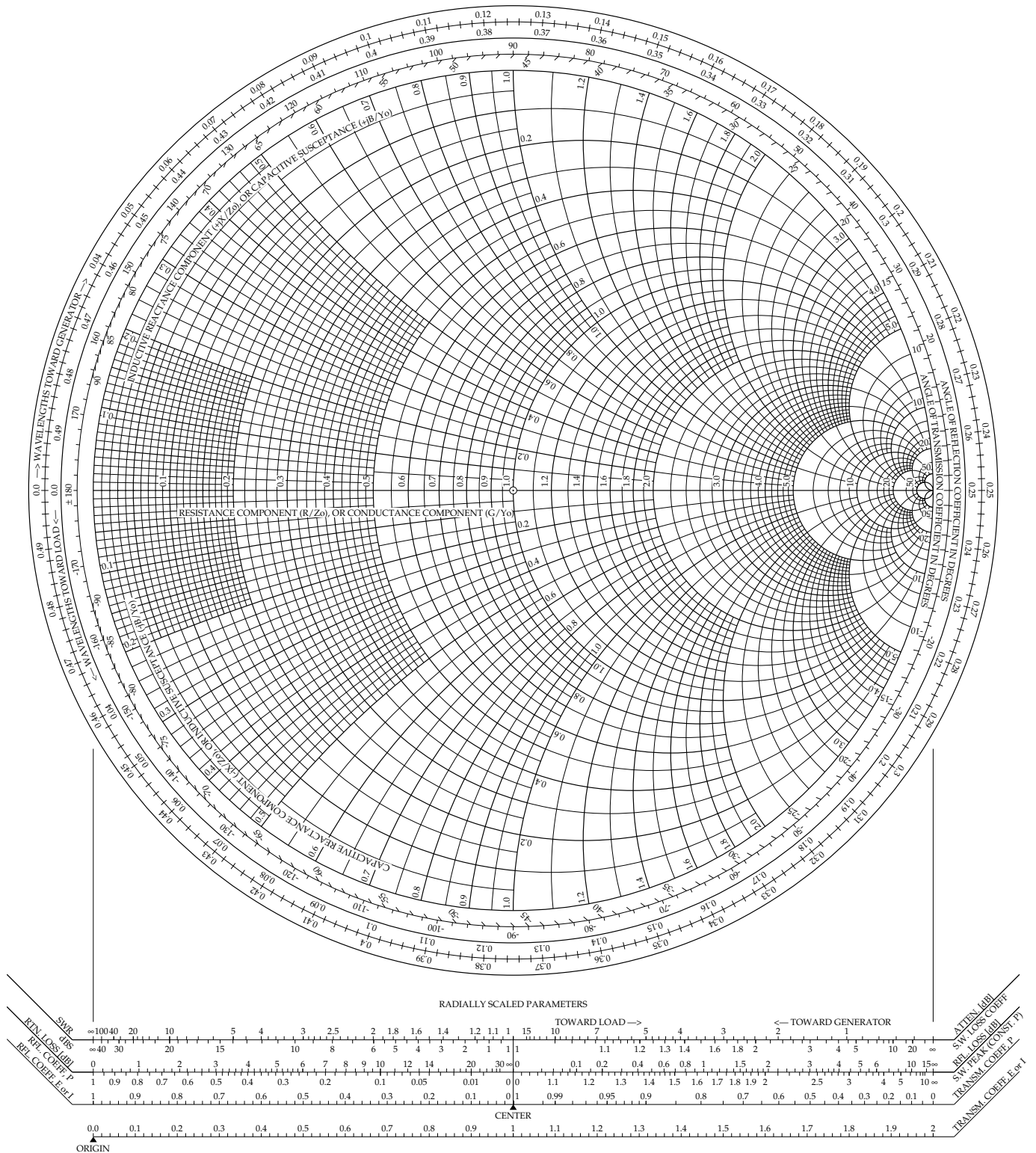

(Source: Wikipedia)

Ex 9-13:

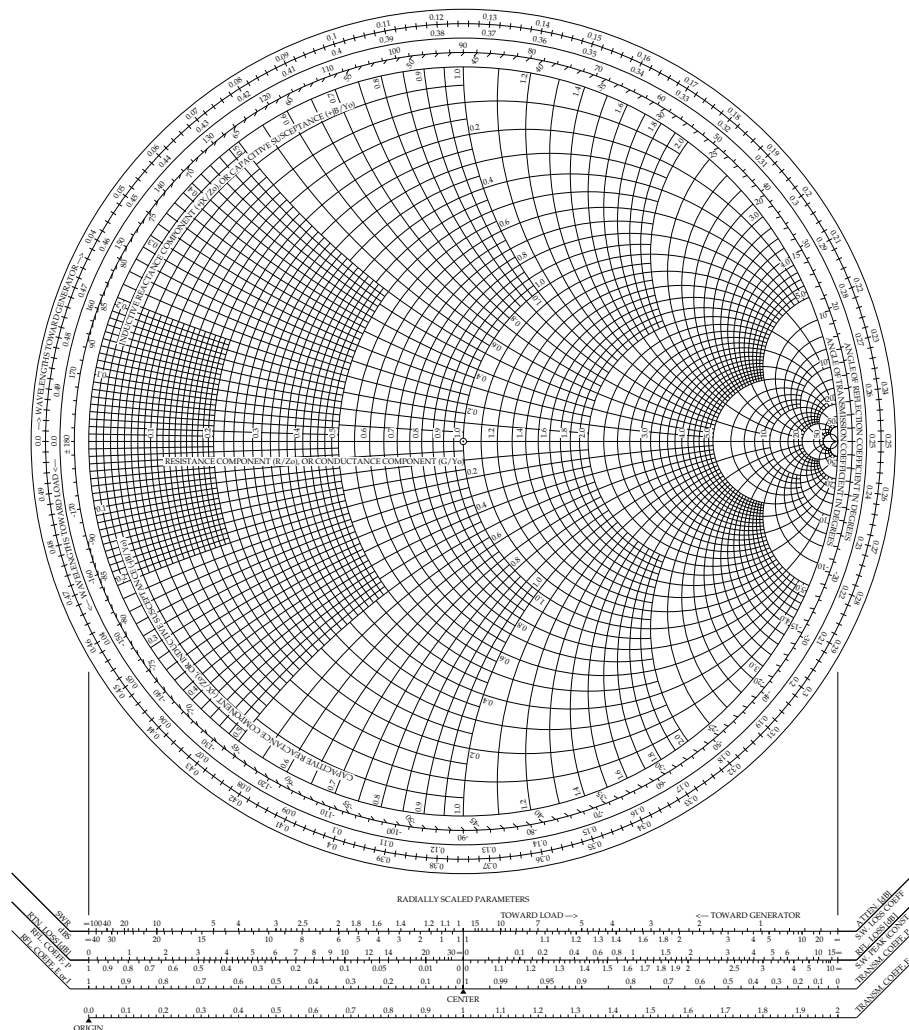
The Complete Smith Chart
Black Magic Design



(Source: Wikipedia)

Ex 9-14:

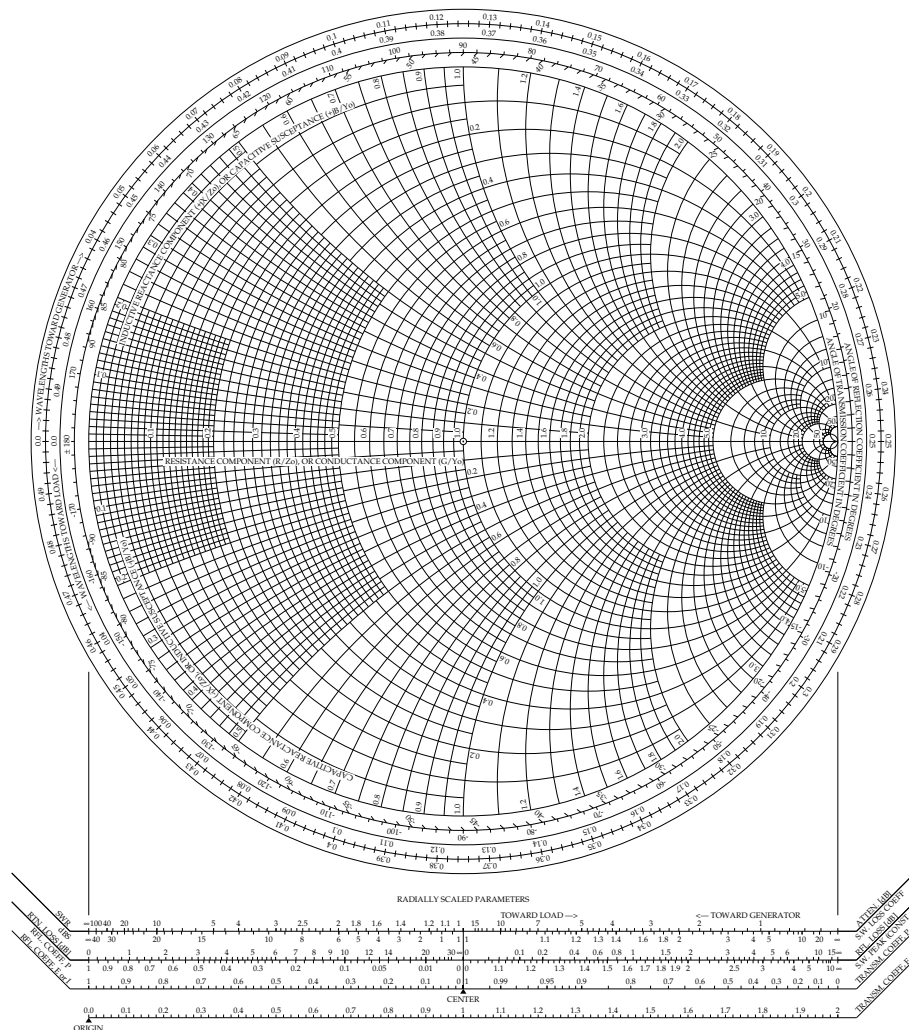
The Complete Smith Chart Black Magic Design



(Source: Wikipedia)

Ex 9-15: Solving Ex 9-9 using Smith Chart

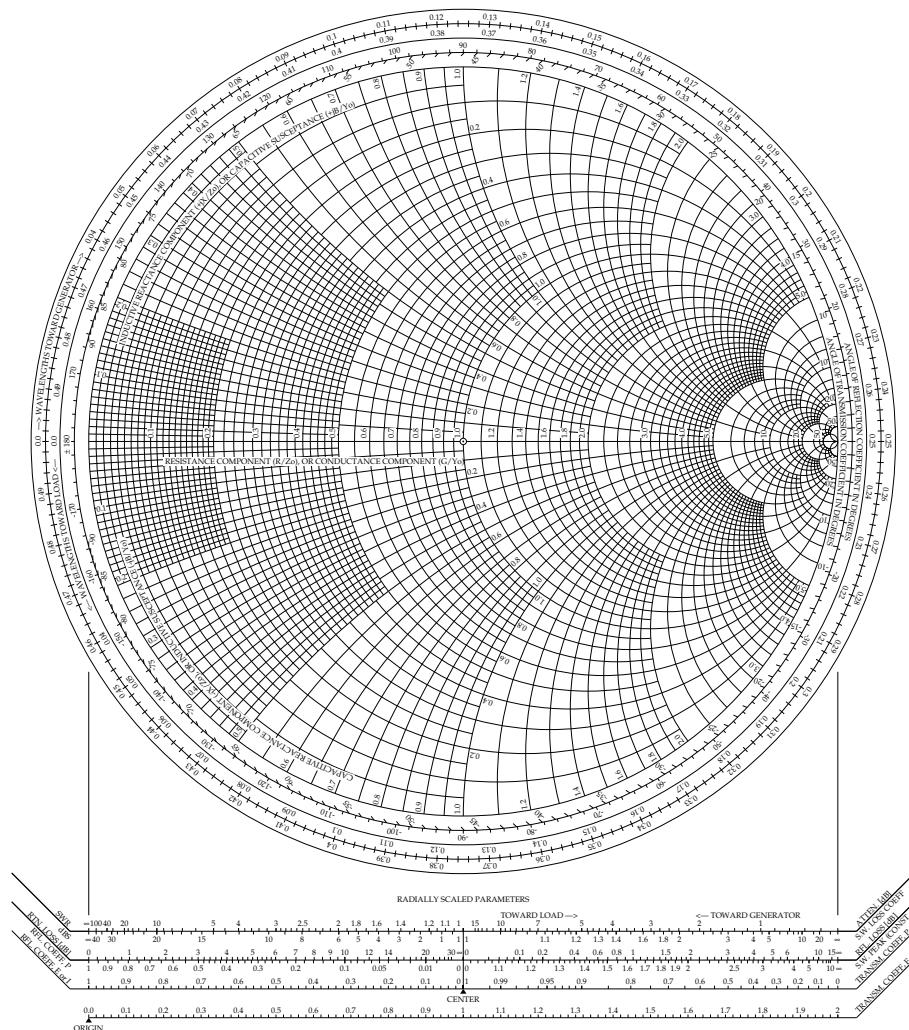The Complete Smith Chart
Black Magic Design



(Source: Wikipedia)

6. Normalized admittance (p. 499)

Smith Chart relates Γ and normalized load impedance $z_L = Z_L/Z_0$.

Now consider the load impedance Y_L . The normalized load impedance can be defined as

On Smith Chart,

- z_L and y_L are opposite to each other on the $|\Gamma|$ -circle.
- Same Smith Chart can be used to relate Γ and z_L , or Γ' and y_L .
- $z_L = r + jx \Leftrightarrow y_L = g + jb$

Ex 9-18: $Z_L = 95 + j20 \Omega$. Find Y_L .

9.7 Transmission Line Impedance Matching

1. reduce reflection and loss
2. improve power transmission efficiency
3. reduce signal interference
4. protect signal generator

9.7.1 Quarter wave transformer

- Frequency sensitive (quarter "wavelength")
- If $R_0, R'_0 = \text{real}$, $\Rightarrow R_L$ must also be real \Rightarrow can not be used to match complex load impedance Z_L

Ex 9-17:

(a) For equal power to R_1 and R_2 ,

(b) Standing wave ratio:

9.7.2 Single stub matching (Stub tuner)

Find ℓ and d such that

In terms of normalized impedance,

But $y_s = g + jb = jb$,

\Rightarrow


\Rightarrow Find d such that

and ℓ such that

Ex 9-20:

The Complete Smith Chart


Black Magic Design

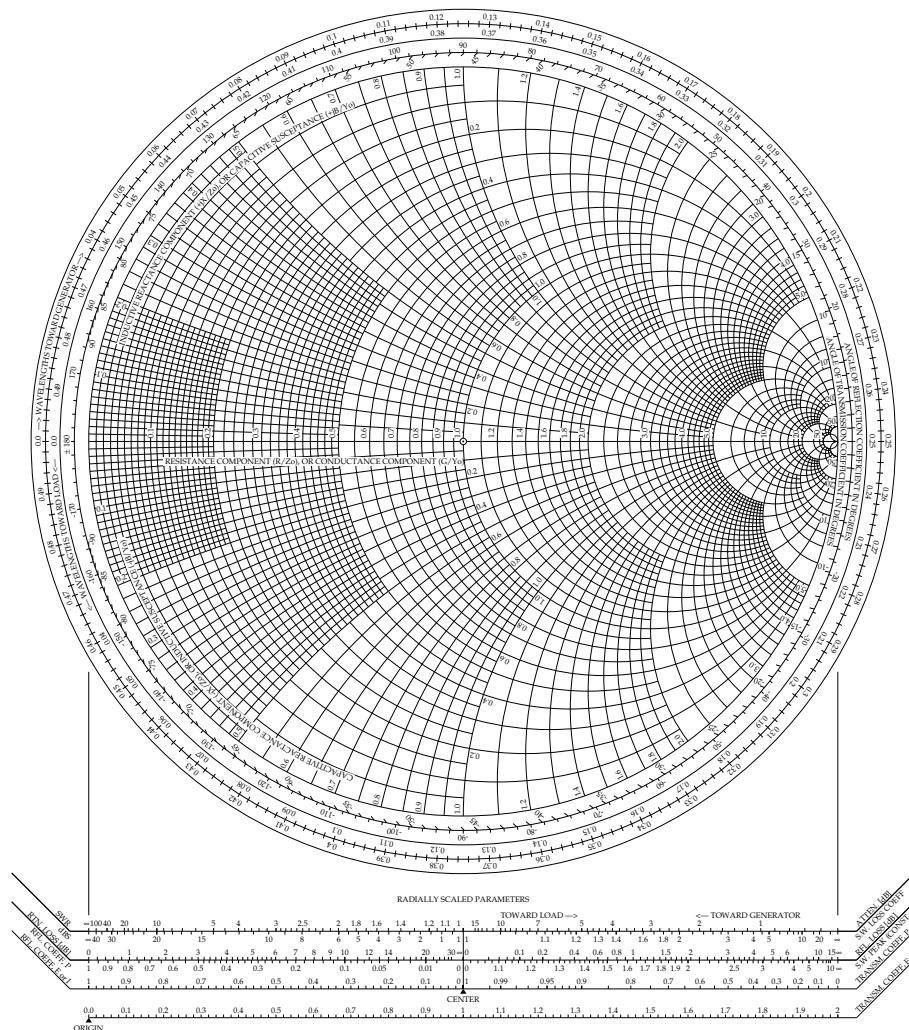

(Source: Wikipedia)

The Complete Smith Chart

Black Magic Design

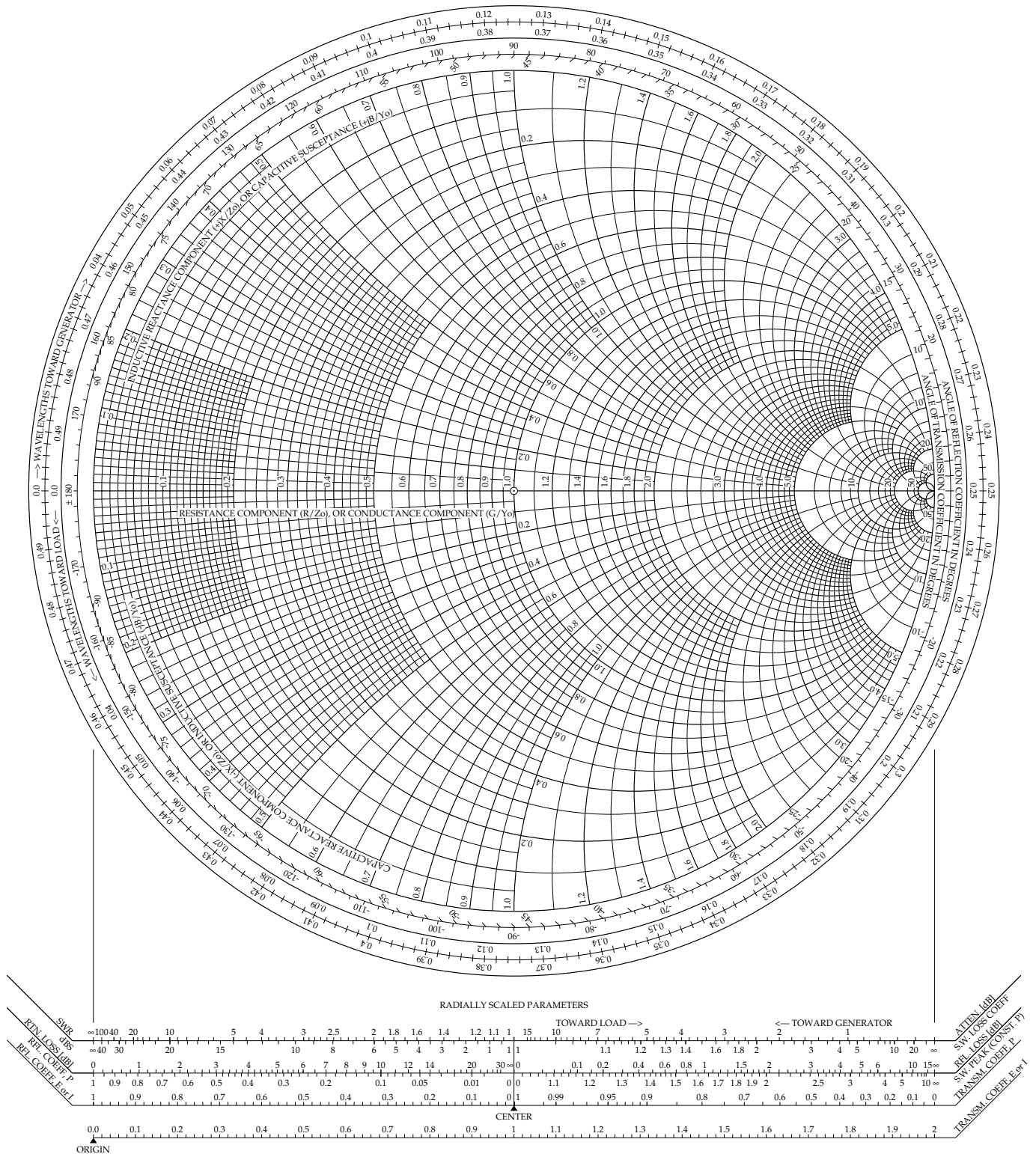

(Source: Wikipedia)

